




The Night Light Challenge

Aaron M. Perez


Dr. P Learning - 2025



In this Lesson...

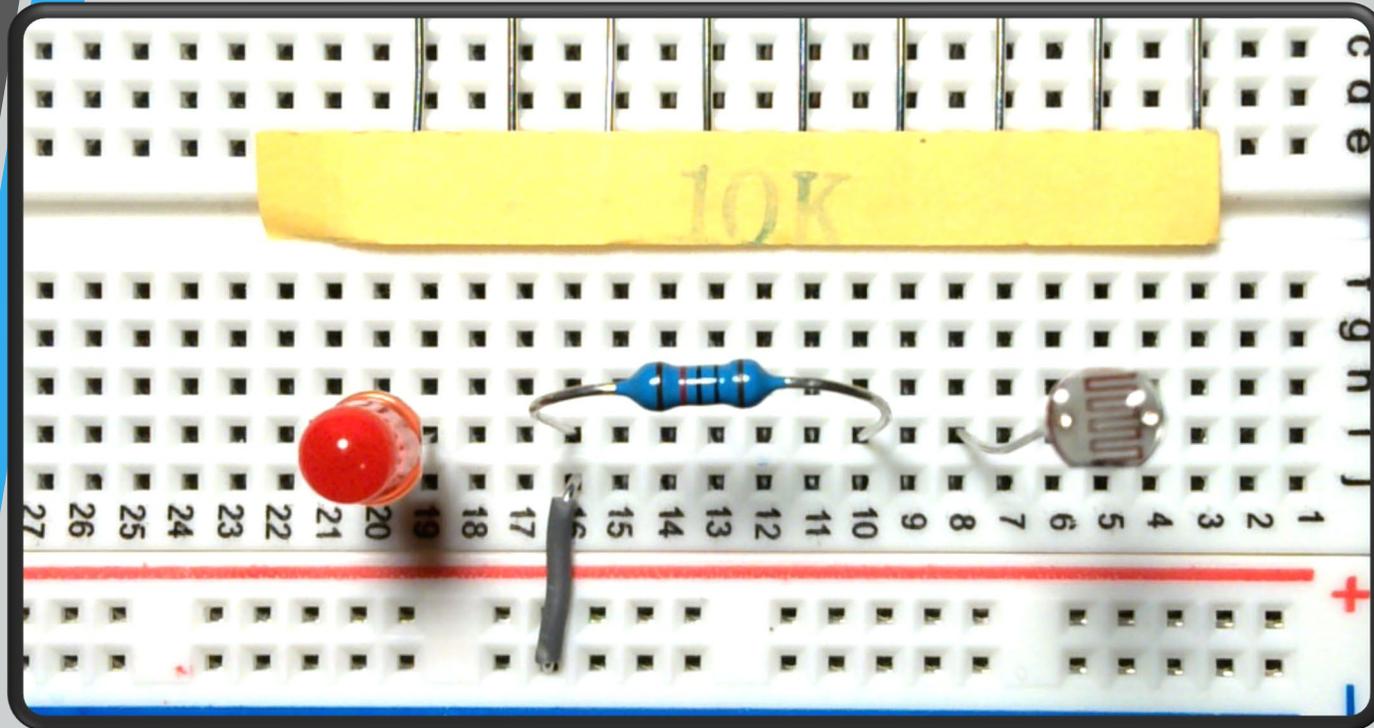
- Students will learn to setup an electrical schematic of a night light using a
 - An LED (Your color choice)
 - A 10 kOhm Resistor (Blue)
 - Photoresistor (light dependent resistor)
 - A pin jumper (gray)
 - Several jumper wires
 - 2 Red
 - 1 Black
 - 1 green



Breadboard

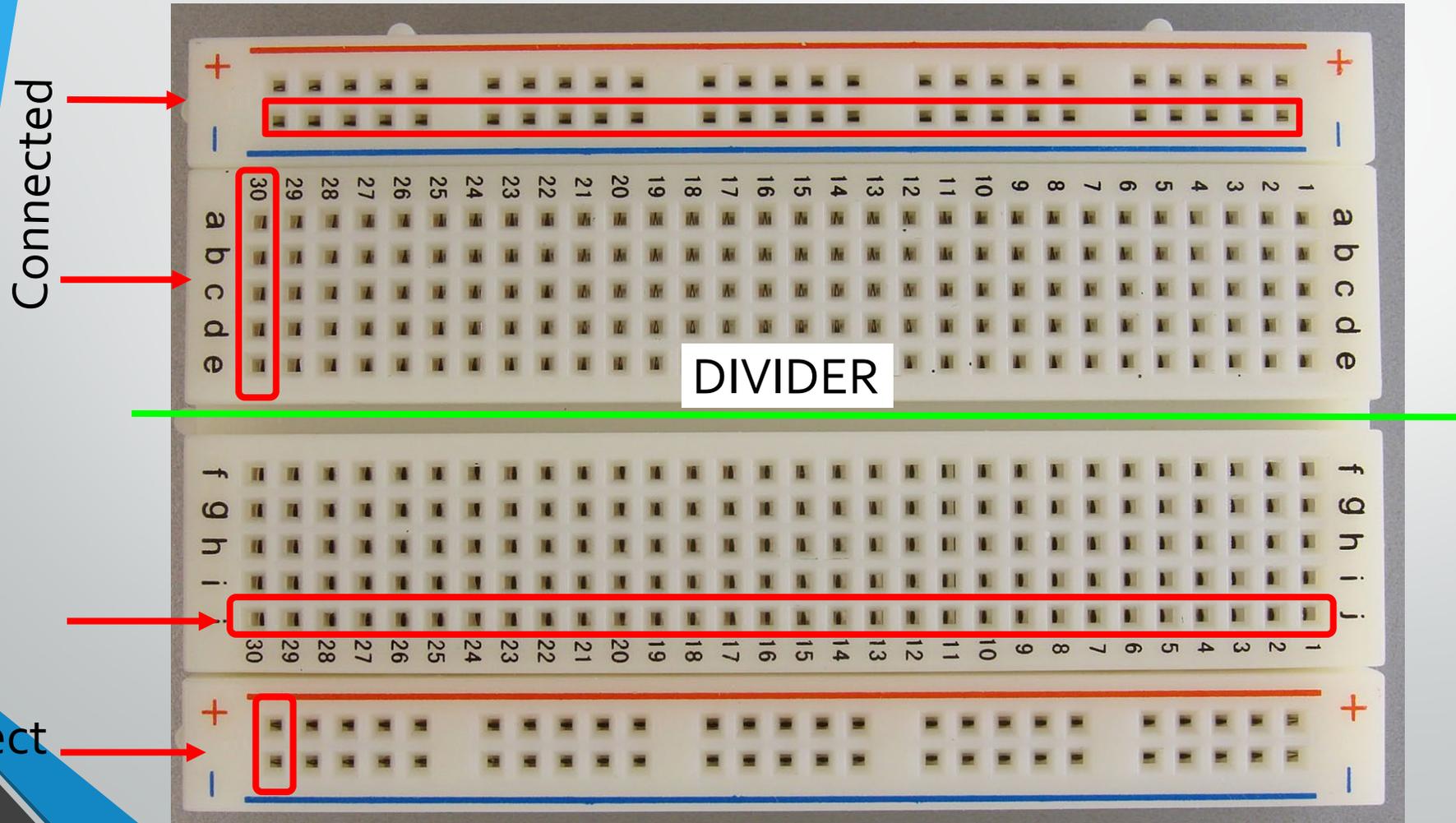

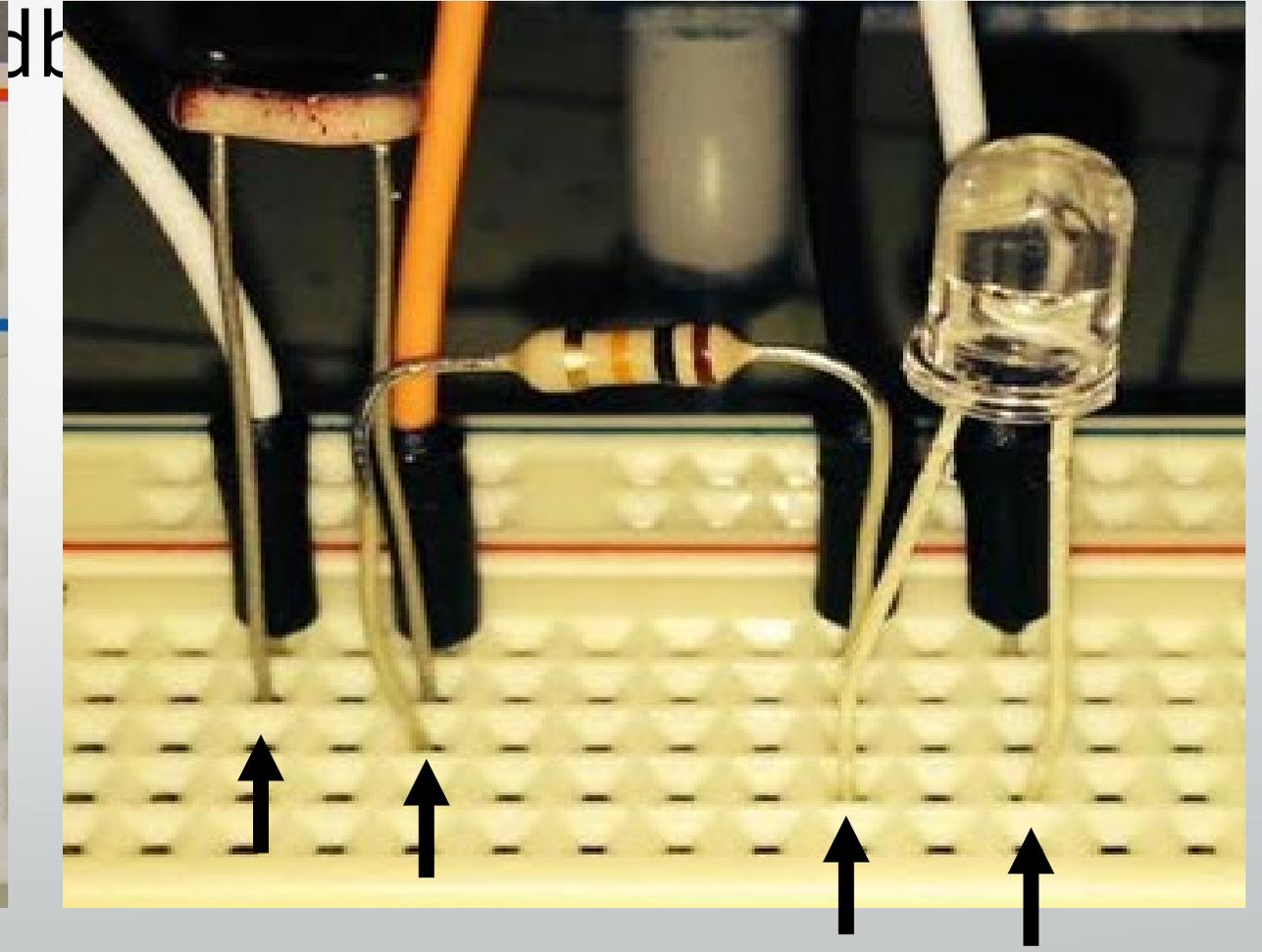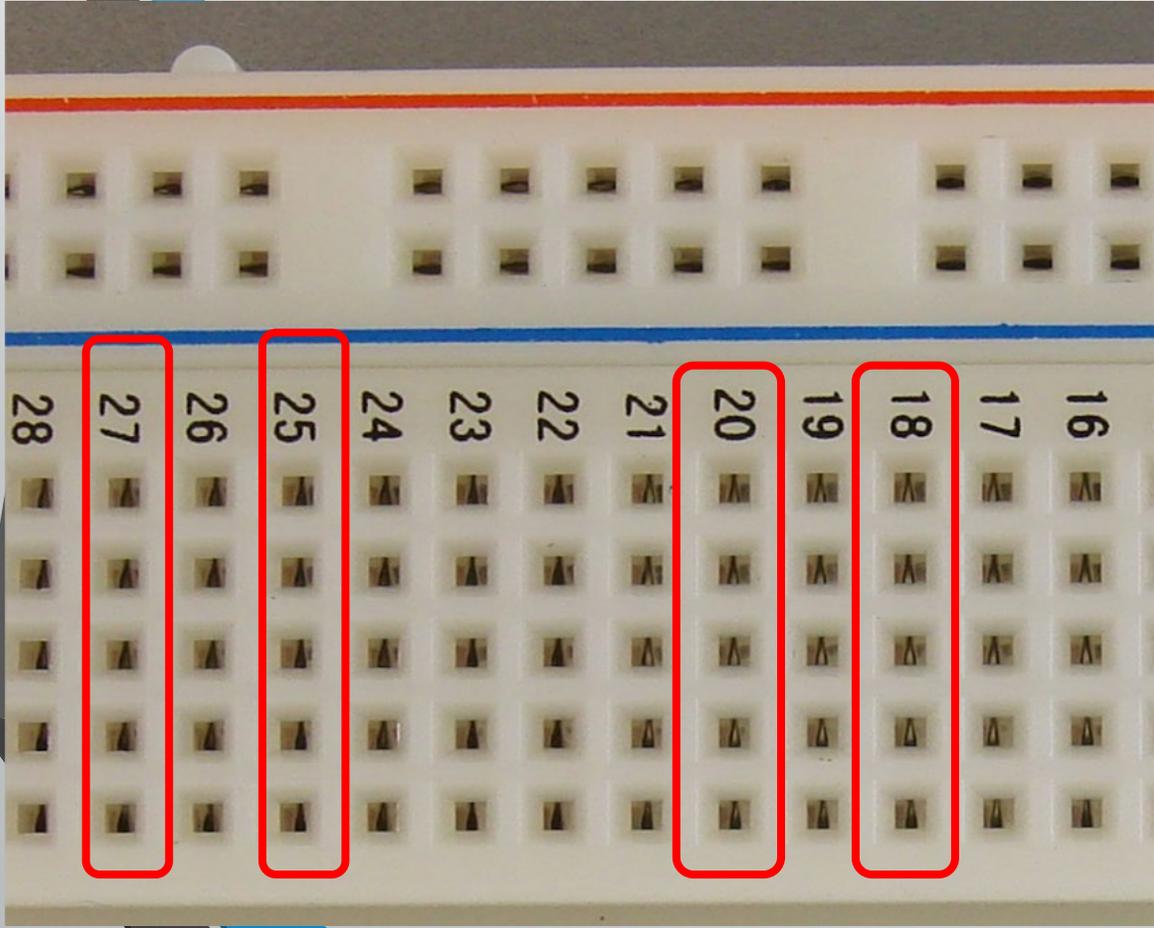


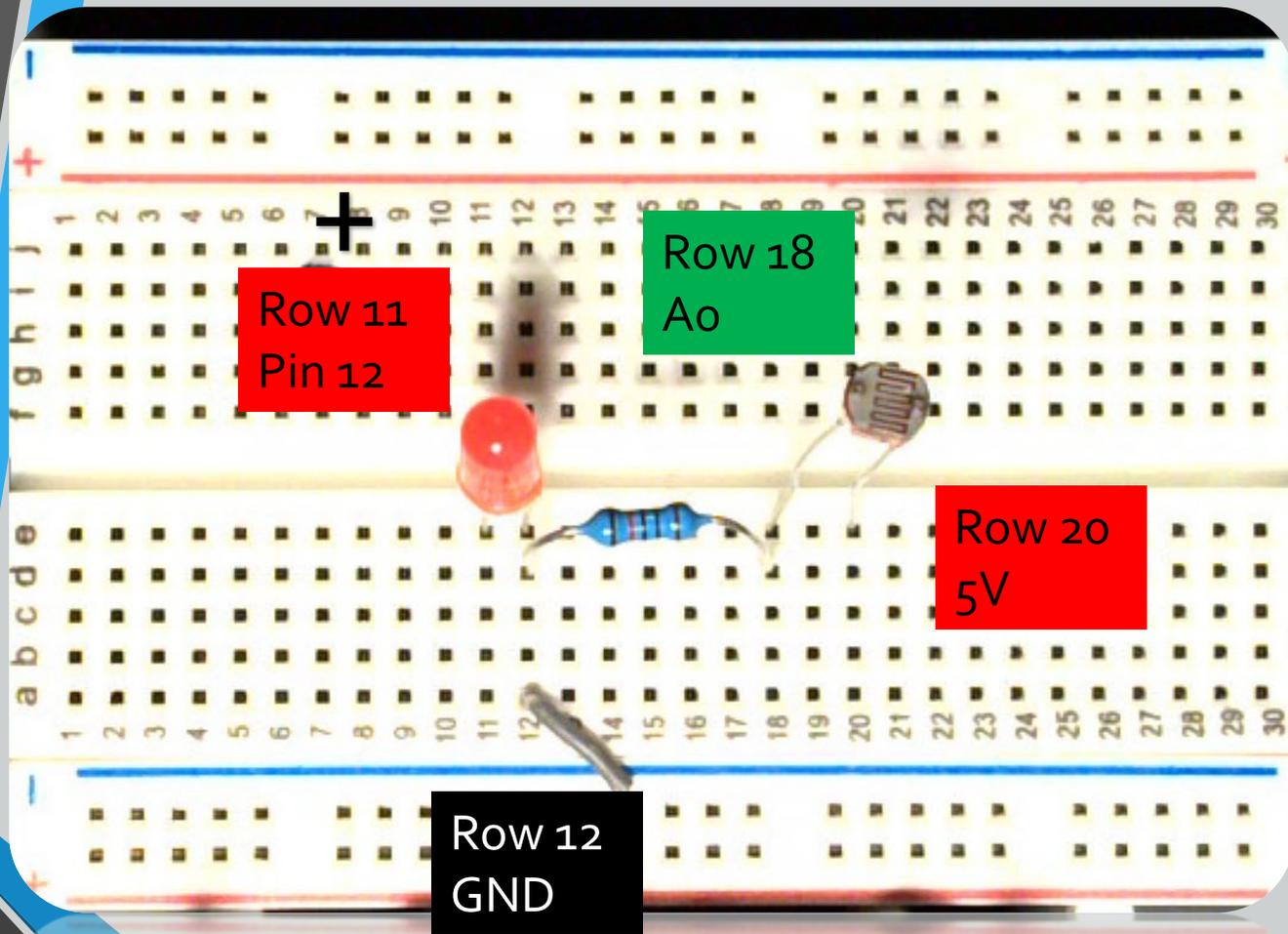

Pause the video here to make sure that you have this setup correctly


- LED
 - Long Stem connected to Pin 12 Power (**Row 11**)
 - Short stem connected to GND with 10 kOhm Resistor (**Row 12**)
- 10 kOhm Resistor
 - Connected to GND with short stem of LED (**Row 12**)
 - Connected to AO with Photoresistor (**Row 18**)
- Photoresistor
 - Connected to AO with 10 kOhm Resistor (**Row 18**)
 - Connected to 5V Power (**Row 20**)

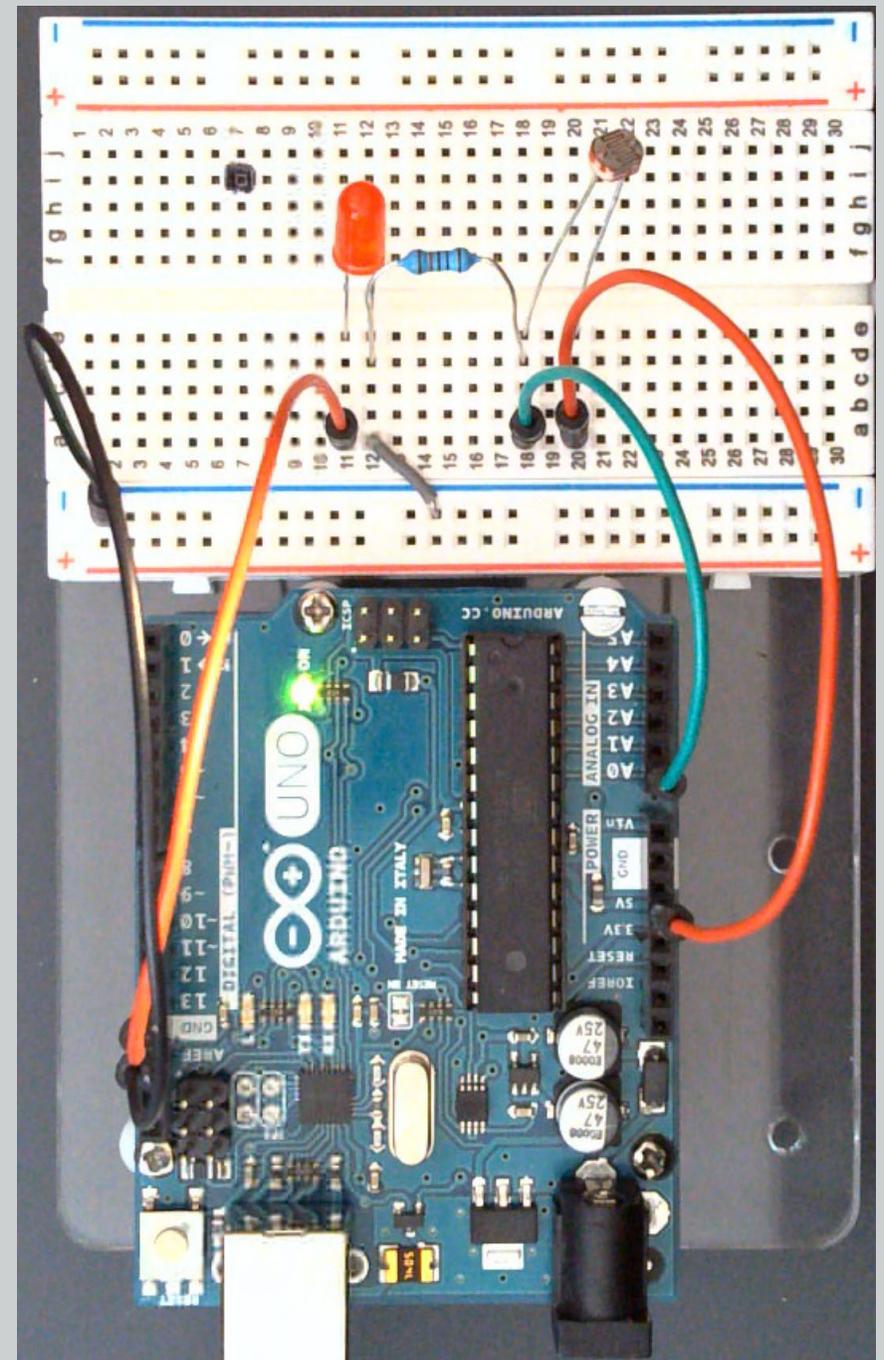- First **Red Wire** to Pin 12 on Arduino and **(+)** column on Breadboard
- **Black Wire** to GND on Arduino and to **(-)** column on Breadboard
- **Green Wire** to **A0** on Arduino and Row 18 on Breadboard
- Second **Red Wire** to 5V on Arduino and Row 20 on Breadboard




Connecting the Jumpers to the Arduino

5V & **A0** (Analog 0)

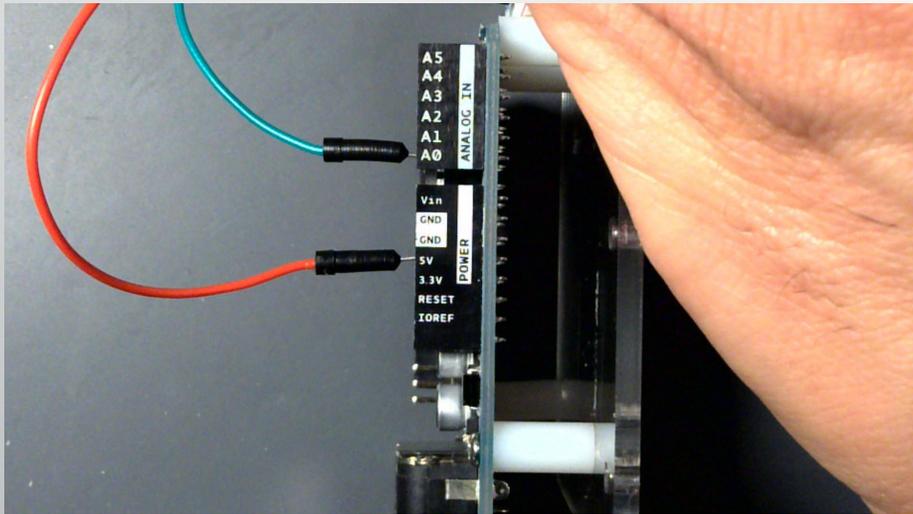


Pin 12 & **GND** (Ground)

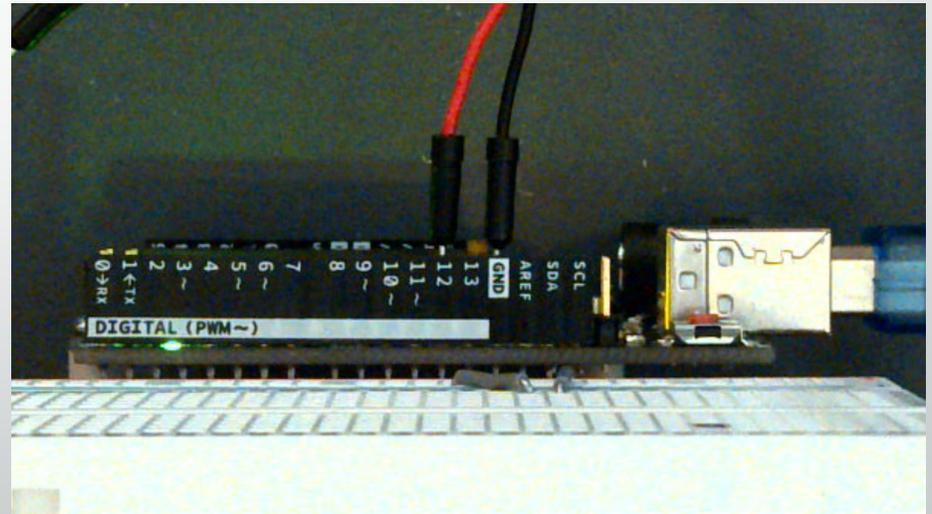

Not Covering the LDR & Covering the LDR

Not covered LDR

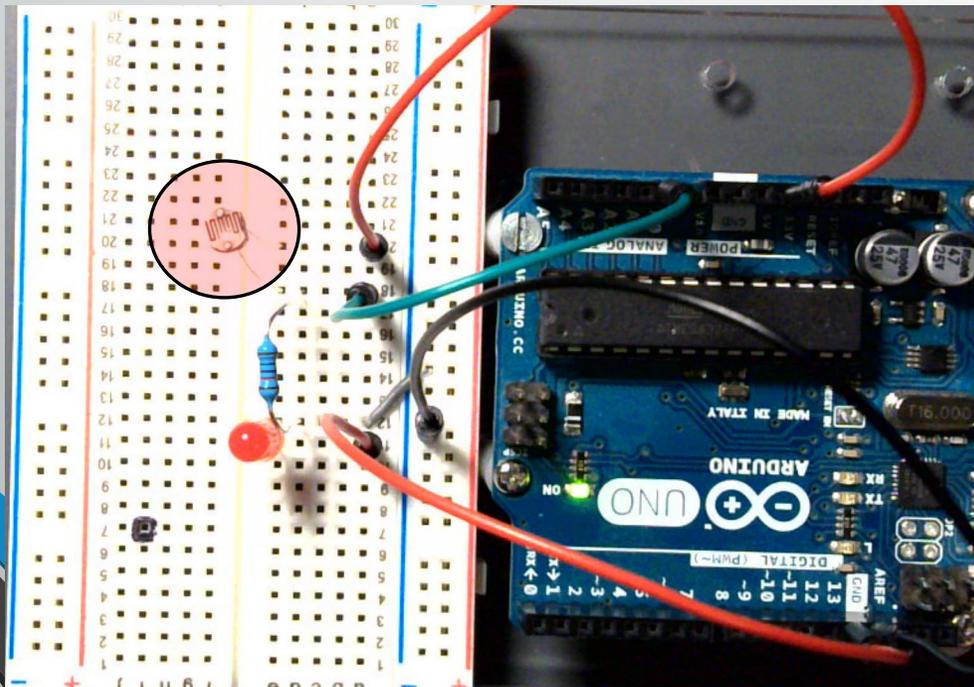

Covered

